

# Experiment -01

## **AIM:**

To simulate and synthesis Logic Gates, Adders and Subtractor using Xilinx ISE.

## **APPARATUS REQUIRED:**

Xilinx 14.7 Spartan6 FPGA

## **PROCEDURE:**

STEP:1 Start the Xilinx navigator, Select and Name the New project.

STEP:2 Select the device family, device, package and speed.

STEP:3 Select new source in the New Project and select Verilog Module as the Source type.

STEP:4 Type the File Name and Click Next and then finish button. Type the code and save it.

STEP:5 Select the Behavioral Simulation in the Source Window and click the check syntax.

STEP:6 Click the simulation to simulate the program and give the inputs and verify the outputs as per the truth table.

STEP:7 Select the Implementation in the Sources Window and select the required file in the Processes Window.

STEP:8 Select Check Syntax from the Synthesize XST Process. Double Click in the Floorplan Area/IO/Logic-Post Synthesis process in the User Constraints process group. UCF(User constraint File) is obtained.


STEP:9 In the Design Object List Window, enter the pin location for each pin in the Loc column Select save from the File menu.

STEP:10 Double click on the Implement Design and double click on the Generate Programming File to create a bitstream of the design.(.v) file is converted into .bit file here.

STEP:11 Load the Bit file into the SPARTAN 6 FPGA

STEP:12 On the board, by giving required input, the LEDs starts to glow light, indicating the output.

## LOGIC GATES: LOGIC DIAGRAM:

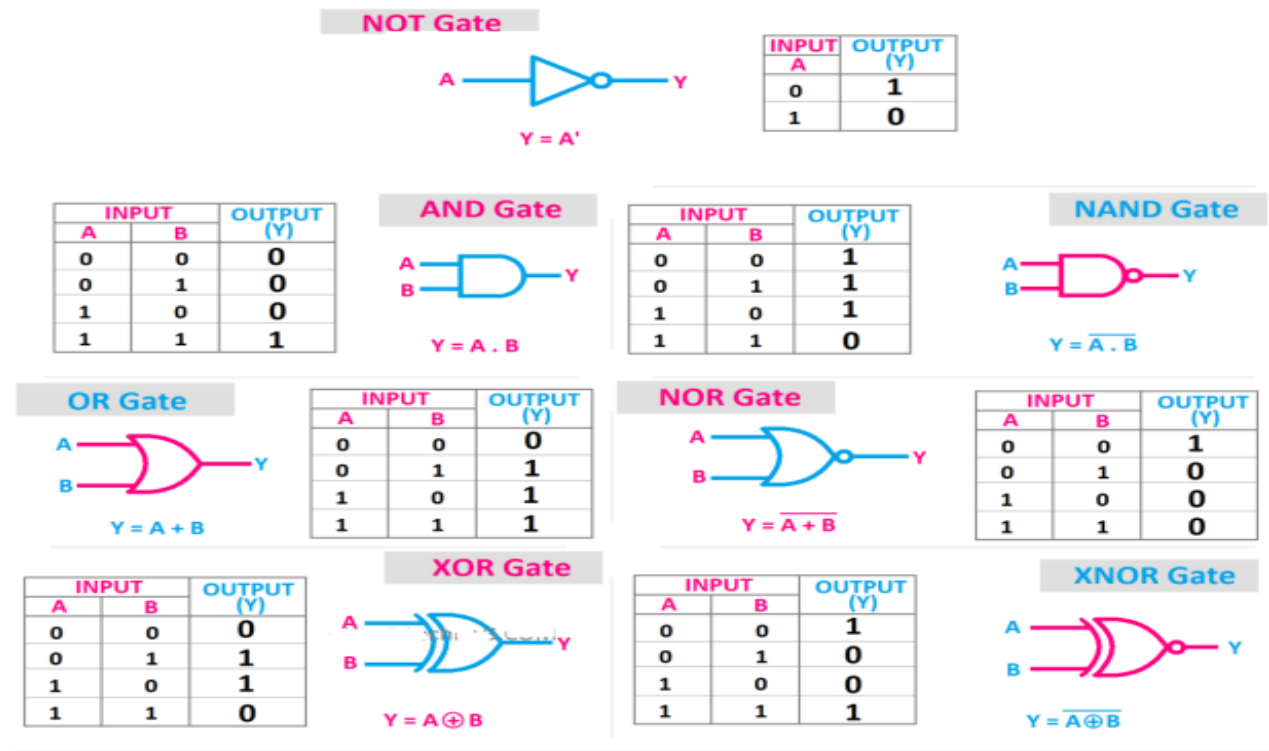

## VERILOG CODE:

```

Module logicgates(a,b,andgate,orgate,xorgate,nandgate,norgate,xnorgate,notgate);
input a,b;
output andgate,orgate,xorgate,nandgate,norgate,xnorgate,notgate;
and(andgate,a,b);
or(orgate,a,b);
xor(xorgate,a,b);
nand(nandgate,a,b);
nor(norgate,a,b);
xnor(xnorgate,a,b);
not(notgate,a);
endmodule


```

OUTPUT:

Name	Value		10,999,986 ps	10,999,988 ps	10,999,990 ps	10,999,992 ps	10,999,994 ps
a	1						
b	1						
w	0						
y	0						
x	1						
c	1						
d	0						
e	1						
f	0						

Half Adder:

LOGIC DIAGRAM:

 


VERILOG CODE:

```
module ha(x,y,a,b);
input x,y;
output a,b;
xor x1(a,x,y);
and x2(b,x,y);
endmodule
```

OUTPUT:

Name	Value	10,999,978 ps	10,999,980 ps	10,999,982 ps	10,999,984 ps	10,999,986 ps	10,999,988 ps	10,999,990 ps	10,999,992 ps	10,999,994 ps	10,999,996 ps	10,999,998 ps
x	1											
y	1											
a	0											
b	1											


Full adder:  
LOGIC DIAGRAM:

 

VERILOG CODE:


```
module fa(a,b,cin,sum,carry);
input a,b,cin;
output sum,carry;
wire w1,w2,w3;
xor x1(w1,a,b);
and x2(w2,a,b);
xor x3(sum,w1,cin);
and x4(w3,w1,cin);
or x5(carry,w3,w2);
endmodule
```

OUTPUT:

 

**Half Subtractor:**


LOGIC DIAGRAM:

 

VERILOG CODE:


```
module hs(x,y,d,b);
input x,y;
output d,b;
wire w;
xor x1(d,x,y);
not n1(w,x);
and a1(b,y,w);
endmodule
```

OUTPUT:

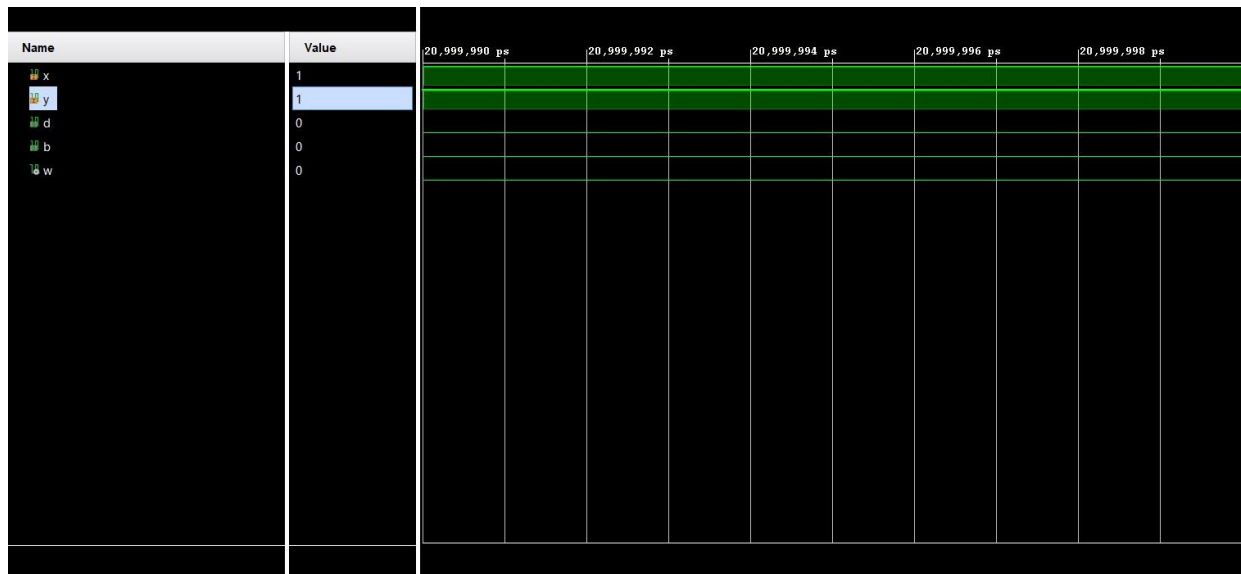

**Full Subtractor:**

LOGIC DIAGRAM:

 


VERILOG CODE:

```

module fs(a,b,cin,d,e);
input a,b,cin;
output d,e;
wire w1,w2,w3,w4,w5;
xor x1(w2,a,b);
not n1(w1,a);
and a1(w4,w1,b);
xor x2(d,w2,cin);
not n2(w3,w2);
and a2(w5,w3,cin);
or o1(e,w5,w4);
endmodule


```

OUTPUT:

 

## 8 Bit Ripple Carry Adder

LOGIC DIAGRAM:

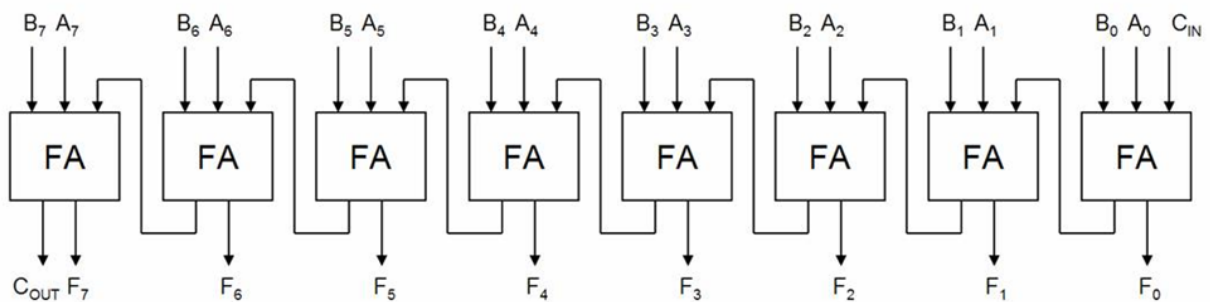


## VERILOG CODE:

```
module fa(a,b,cin,sum,carry);
input a,b,cin;
output sum,carry;
wire w1,w2,w3;
xor x1(w1,a,b);
and x2(w2,a,b);
xor x3(sum,w1,cin);
and x4(w3,w1,cin);
or x5(carry,w3,w2);
endmodule
```

```
module rca(a,b,cin,sum,carry);
input [3:0]a,b;
input cin;
output[3:0]sum;
output carry;
wire w1,w2,w3;
fa g1(.a(a[0]),
      .b(b[0]),
      .cin(cin),
      .s(sum[0]),
      .carry(w1)
    );
fa g2(.a(a[1]),
      .b(b[1]),
      .cin(w1),
      .s(sum[1]),
      .carry(w2)
    );
fa g3(.a(a[2]),
      .b(b[2]),
      .cin(w2),
      .s(sum[2]),
      .carry(w3)
    );
fa g4(.a(a[3]),
      .b(b[3]),
      .cin(w3),
      .s(sum[3]),
      .carry(carry)
    );
endmodule
```



OUTPUT:

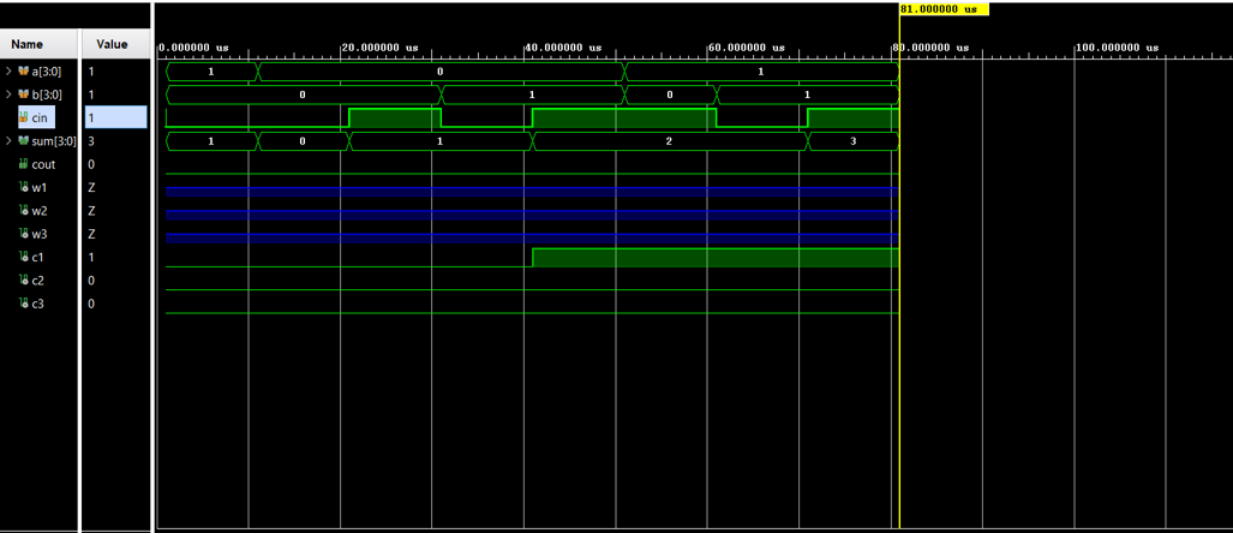

RESULT:

Thus ,the given logic gates,half adder,full adder,half subtractor are simulated and synthesis are excuted successfully .